 




# ***Electronic design - some practicalities***

- R, L, C & PCBs - non-ideal behaviour
- opamps
- power management
- I2C
- packages
- DACs
- loading
- spectrum analyser
- bypass C, filters



  
# PCB tracks & layout

- **not** zero Ohms, zero Farads, zero Henrys



 
# PCB tracks & layout

- So,
- generous track width
- route power intelligently
- close to ground, away from data, small signal
- use groundplanes - sustainability, EMI, EMR



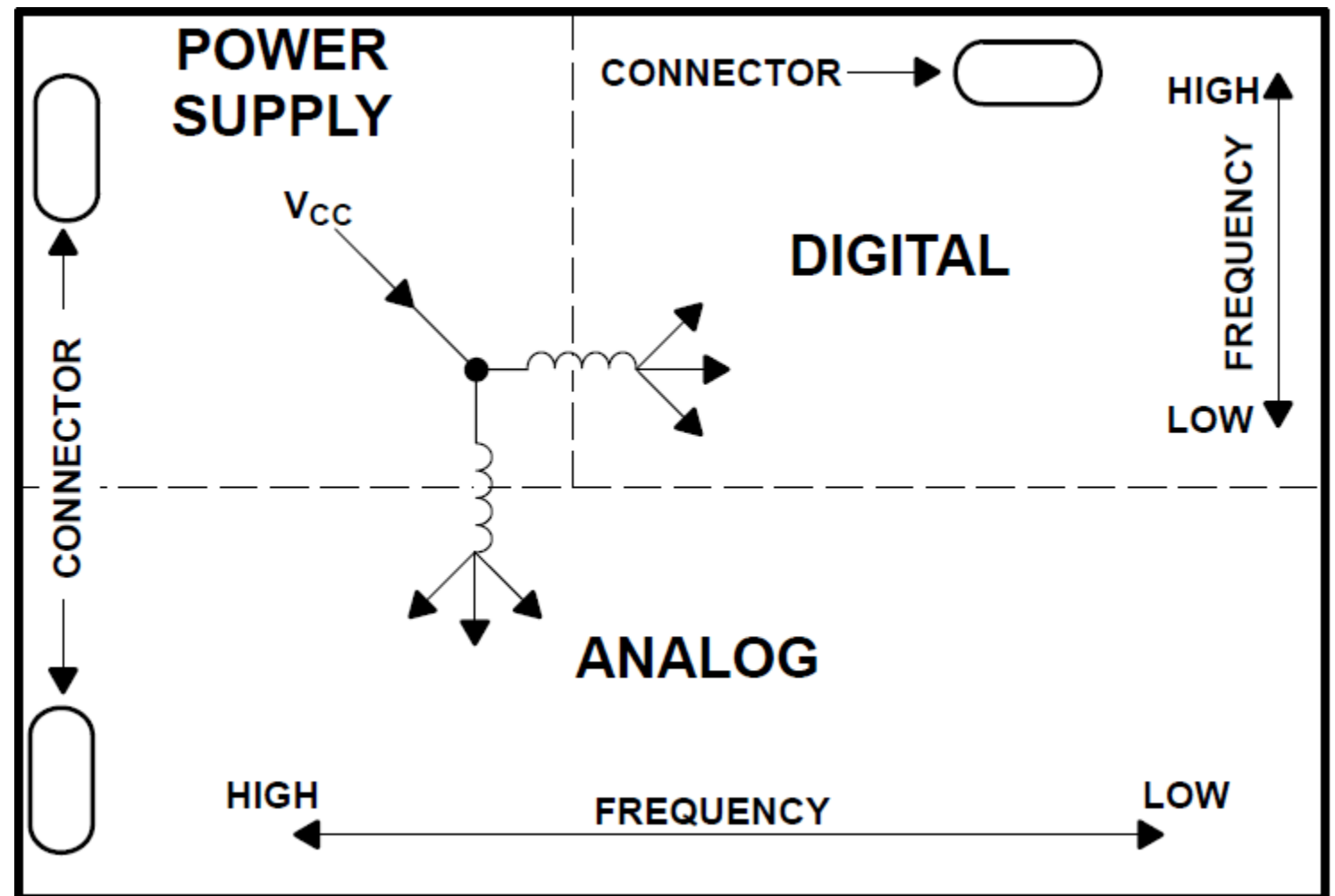
# PCB tracks & layout

- Cluster functional elements
- 'Star' grounding avoids ground loops



# Ideal Op Amp

 


1) 
$$v_o = A_v (v_+ - v_-)$$

The open-loop gain,  $A_v$ , is very large, approaching infinity.

2) 
$$i_+ = i_- = 0$$

The current into the inputs are zero.


# Ideal Op Amp with Negative Feedback

 

## Golden Rules of Op Amps:

1. The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
2. The inputs draw no current.

# Non-inverting Amplifier

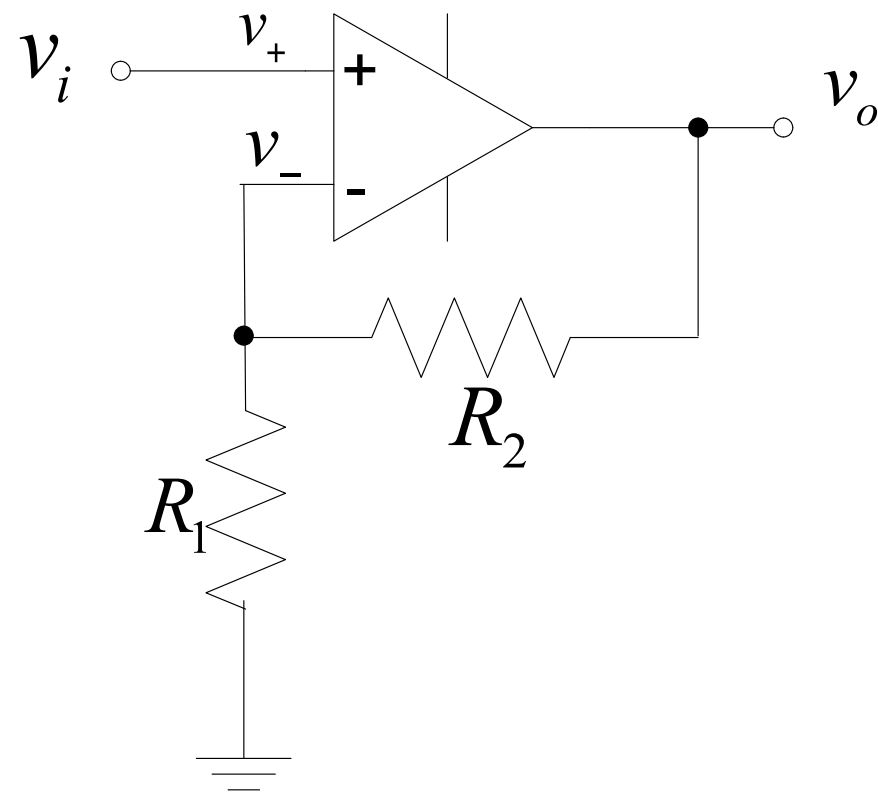


Closed-loop voltage gain

$$A_F = \frac{v_o}{v_i}$$

$$v_i = v_+ = v_- = \frac{R_1}{R_1 + R_2} v_o$$

$$A_F = \frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$

# Unity-Gain Buffer

 

Closed-loop voltage gain

$$A_F = \frac{v_o}{v_i}$$

$$v_i = v_+ = v_- = v_o$$


$$A_F = \frac{v_o}{v_i} = 1$$

Used as a "line driver" that transforms a high input impedance (resistance) to a low output impedance. Can provide substantial current gain.



# Inverting Amplifier

Current into op amp is zero

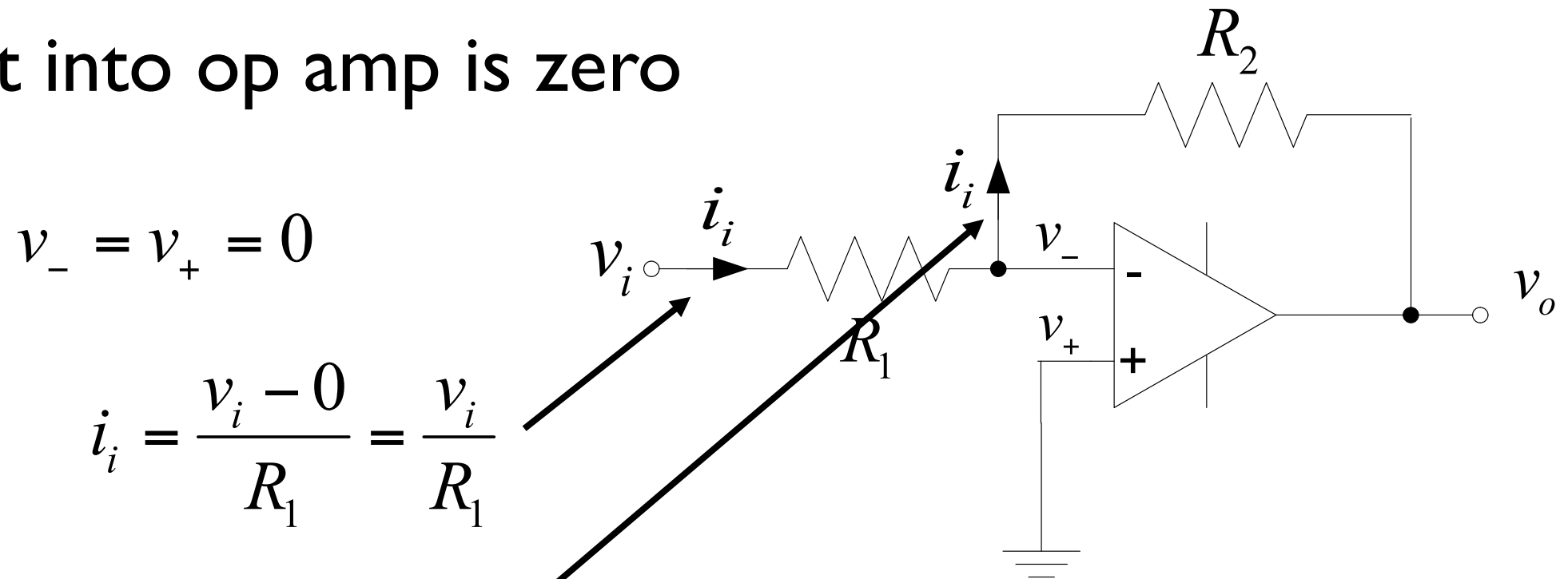


$$i_i = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$$

$$i_i = \frac{0 - v_o}{R_2} = \frac{-v_o}{R_2}$$

$$\frac{v_i}{R_1} = \frac{-v_o}{R_2}$$

$$A_F = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$


# Mixing Amplifier

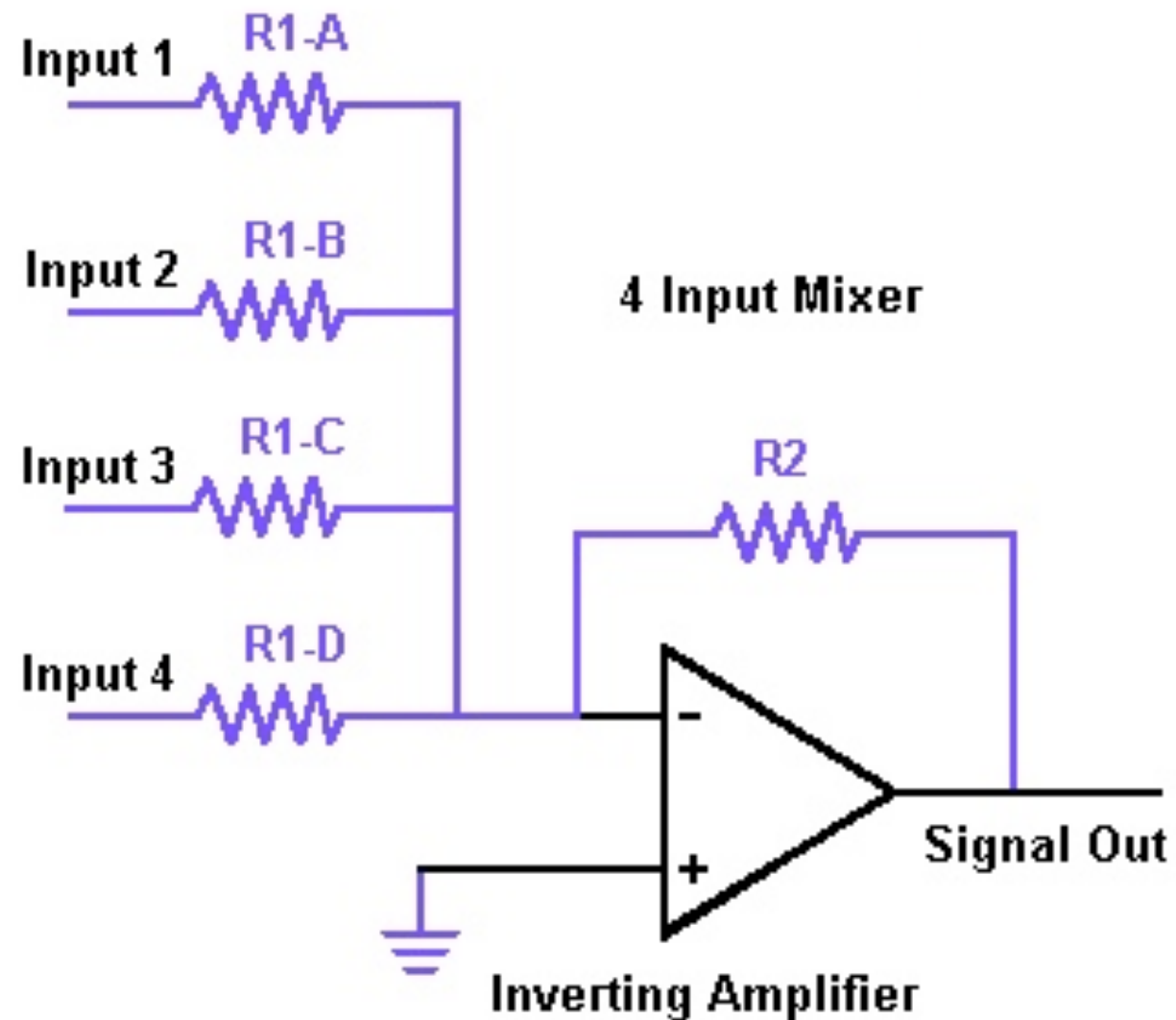

Consider



- equal values of R1
- Inverting Amplifier (or not)
- handle the output 'swing'

# Practical circuit

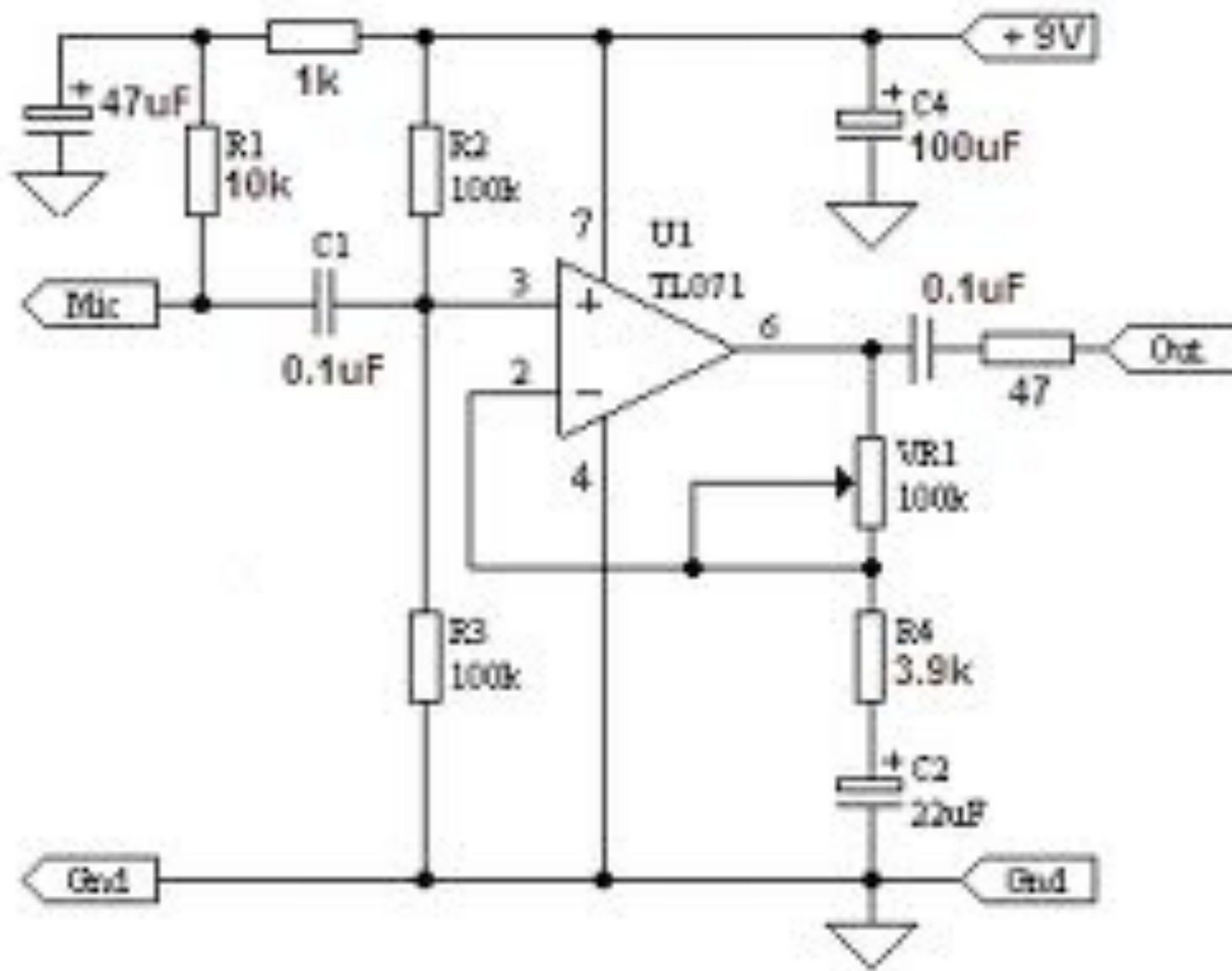

- NOTE
- single supply
- bias
- decoupling
- power line filter cap
- AC coupling

# Power management

  



- **Linear**
- 3 terminal regulators
- 7805, 7905
- LDO types
- EFFICIENCY

Consider:

9 volt battery, 5 volt rail, 100mA draw, 7805 device

4 volt drop @ 100 mA = 400mW loss as HEAT

# Power management

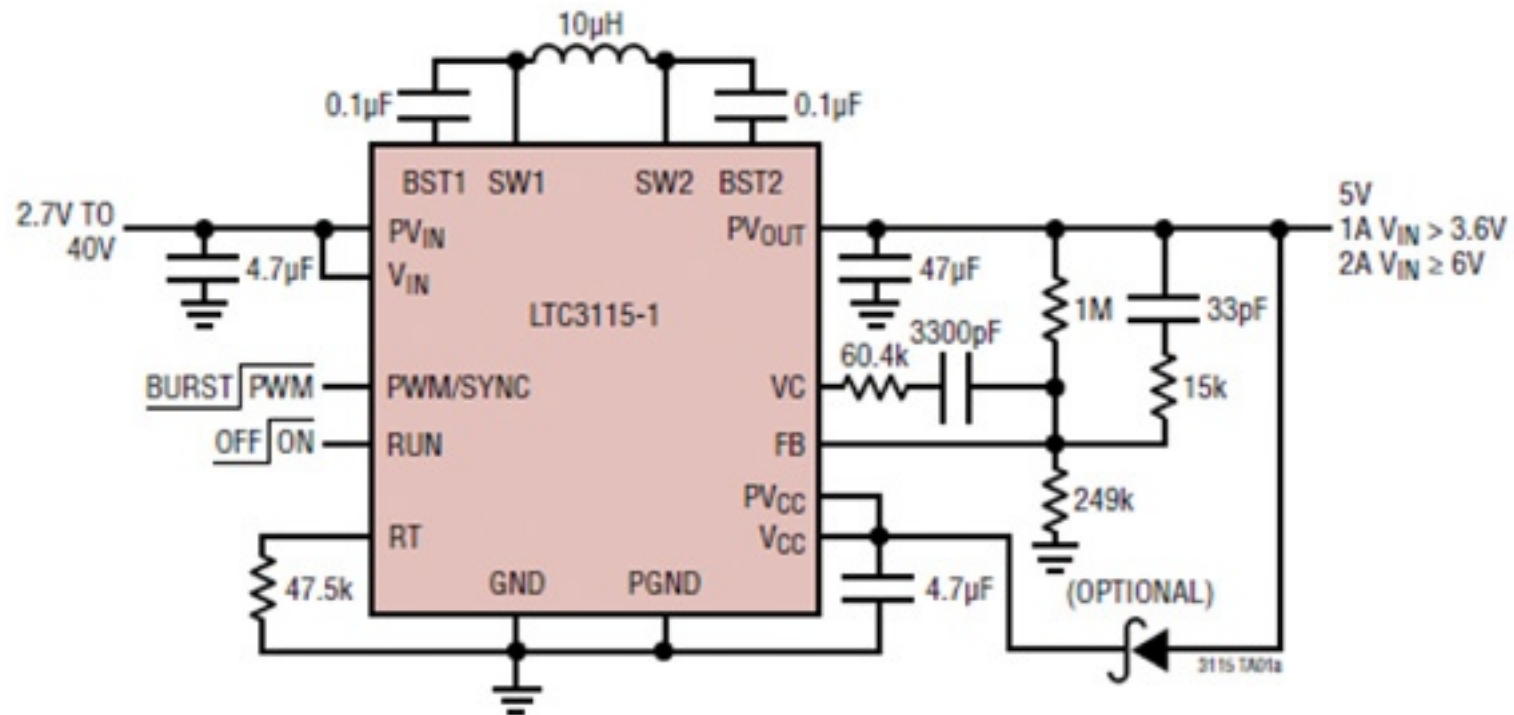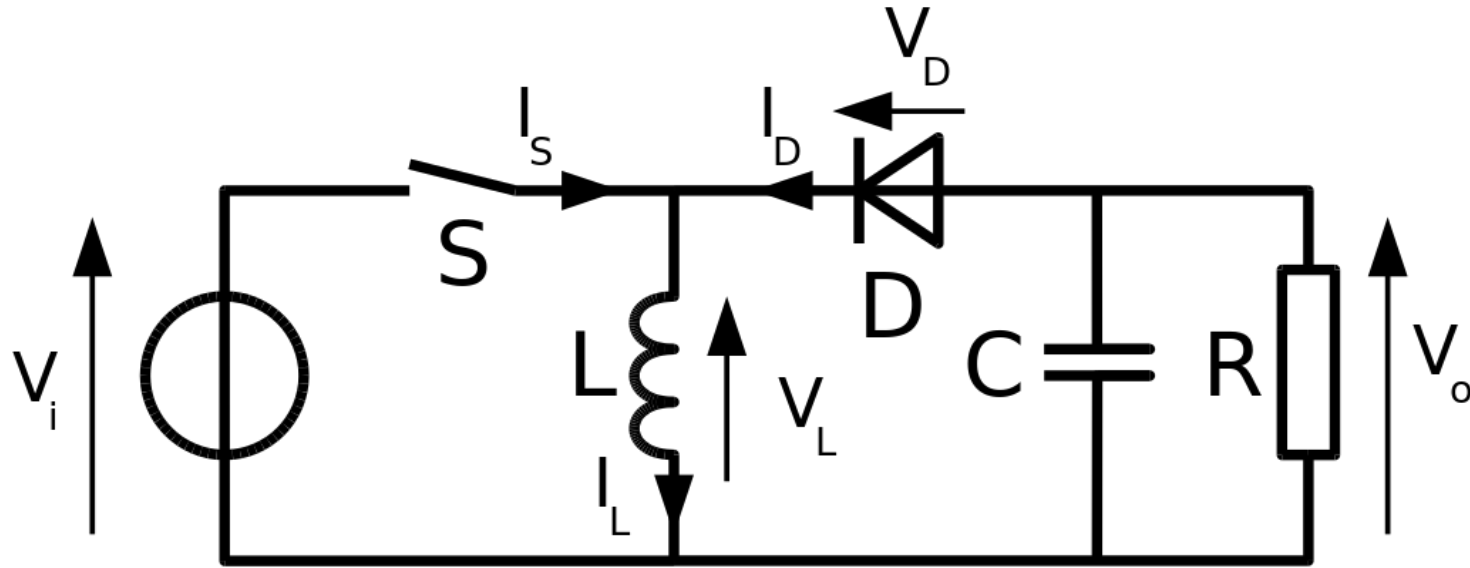

- **SMPS**
- **efficiency** at what voltages/currents?
- **many types!**
- **C and L**
- **tailor  $V_{out}$**

# Why?

- Parallel bus alternatives failing
- Commercial imperatives




# What?

- Inter IC Communications (I2C, “I squared C”)
- “Two Wire”, TWI
- Philips Semiconductors (now NXP)
- Defined in **UM10204** I2C-bus specification and user manual
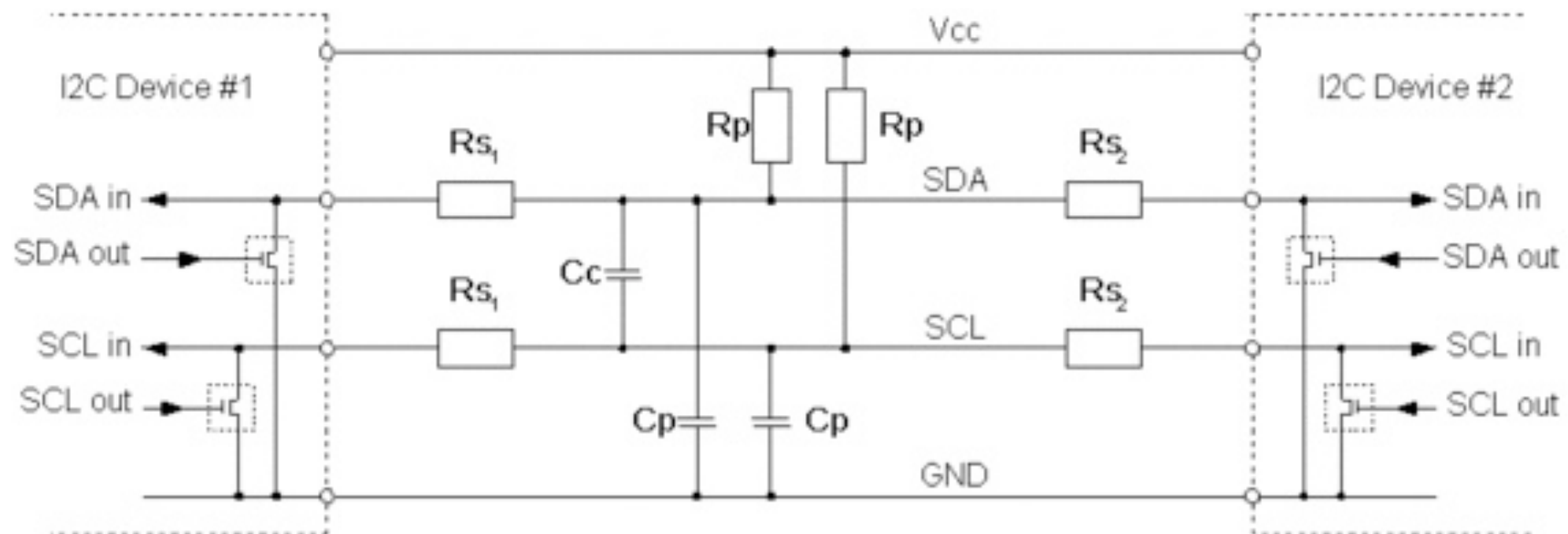
# How?


- Two wires - data and clock (SDA, SCL)
- Defined ICs have a fixed (8 bit) address






# How?

- Master & (multiple) slaves

 

# Basic Command Structure

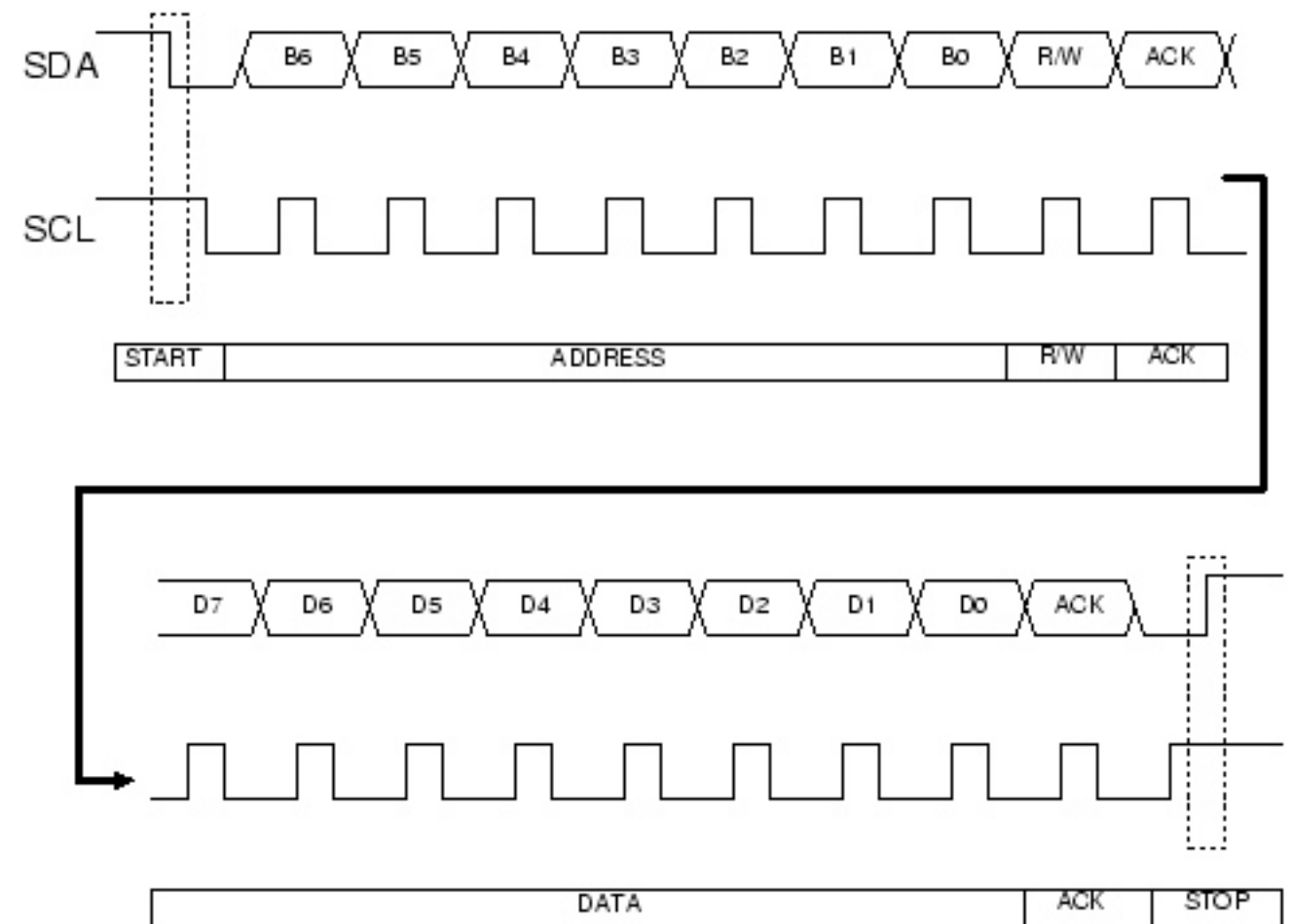1. Send the START bit (S).
- 2. Send the slave address (ADDR).
- 3. Send the Read(R)-1 / Write(W)-0 bit.
- 4. Wait for/Send an acknowledge bit (A).
- 5. Send/Receive the data byte (8 bits) (DATA).
- 6. Expect/Send acknowledge bit (A).
- 7. Send the STOP bit (P).



# What is the correct address?



Figure 3. Slave Address Bits

## CAT24C512

### 512 kb I<sup>2</sup>C CMOS Serial EEPROM

#### Description

The CAT24C512 is a 512 kb Serial CMOS EEPROM, internally organized as 65,536 words of 8 bits each.

It features a 128-byte page write buffer and supports the Standard (100 kHz), Fast (400 kHz) and Fast-Plus (1 MHz) I<sup>2</sup>C protocol.

Write operations can be inhibited by taking the WP pin High (this protects the entire memory).

External address pins make it possible to address up to eight CAT24C512 devices on the same bus.


#### Features

- Supports Standard, Fast and Fast-Plus I<sup>2</sup>C Protocol
- 1.8 V to 5.5 V Supply Voltage Range
- 128-Byte Page Write Buffer
- Hardware Write Protection for Entire Memory
- Schmitt Triggers and Noise Suppression Filters on I<sup>2</sup>C Bus Inputs (SCL and SDA)
- Low Power CMOS Technology
- 1,000,000 Program/Erase Cycles
- 100 Year Data Retention
- Industrial and Extended Temperature Range
- 8-pin PDIP, SOIC, TSSOP, MSOP and 8-pad UDFN Packages
- These Devices are Pb-Free, Halogen Free/BFR Free and are RoHS Compliant




ON Semiconductor®

<http://onsemi.com>

 

#### PIN CONFIGURATION

 

- selectable address for this IC
- NB: READ/WRITE bit
- data read (or written) in 8 bit packets with the clock.

# Basics of using an I2C IC (EEPROM)

 


Figure 3. Slave Address Bits

 


Figure 11. Selective Read Timing


example above is for reading back one byte only.

# Component packages

 
## TL071, TL071A, TL071B, TL072 TL072A, TL072B, TL074, TL074A, TL074B LOW-NOISE JFET-INPUT OPERATIONAL AMPLIFIERS

SLOS080D – SEPTEMBER 1978 – REVISED AUGUST 1996


TL071, TL071A, TL071B  
D, JG, P, OR PW PACKAGE  
(TOP VIEW)



 
TL072, TL072A, TL072B  
D, JG, P, OR PW PACKAGE  
(TOP VIEW)




TL074, TL074A, TL074B  
D, J, N, OR PW PACKAGE  
TL074...W PACKAGE  
(TOP VIEW)

 



TL071  
FK PACKAGE  
(TOP VIEW)

 



TL072  
FK PACKAGE  
(TOP VIEW)

 

TL074  
FK PACKAGE  
(TOP VIEW)

 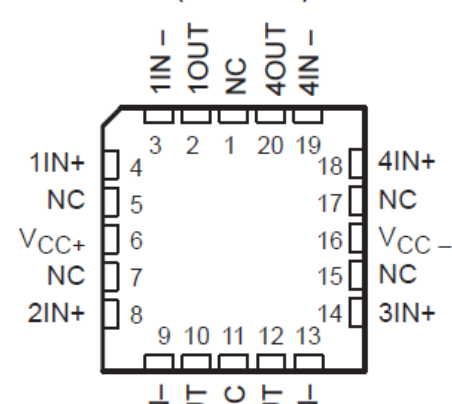

# Component packages

  

**Resistors** - axial, 600 mW, 0.4 inch, 400 mils

**Capacitors** - axial or radial, 0.1 inch, 100 mils - >400 mils - CHECK FIRST